

1. Calculating the total resistance in ohms:
 - a. 100
 - b. 12.5
2. Calculating the total current from the power supply
 - a. 1.25
 - b. 10
3. Calculating the current through each resistor
 - a. 1.25
 - b. 10
4. Calculating the voltage drop through each resistor
 - a. 125
 - b. 125
5. Calculating the power dissipated through each resistor
 - a. 78.125
 - b. 312.5